

Name _____

Enrollment No. _____

Jaypee Institute of Information Technology, Noida

T-2 Examination, EVEN 2023

B. Tech IV Semester

Course Title: Digital Systems

Course Code: 18B11EC213

Maximum Time: 1 Hr

Maximum Marks: 20

CO1: Familiarize with the fundamentals of number system, Boolean algebra and Boolean function minimization techniques.
 CO2: Analyze and design combinational circuit using logic gates.
 CO3: Analyze state diagram and design sequential logic circuits using flip flops.
 CO4: Understand the classification of signals and systems and learn basic signal operations and Fourier analysis.
 CO5: Understand various steps involved in digitization and transmission of signal.

Note: Attempt all questions. All questions are compulsory.

Q. 1 Convert D flip flop in to JK flip flop.


[CO3, 4]

Q. 2 Design a 2-bit magnitude comparator using 1-bit magnitude comparator.

[CO2, 4]

Q. 3 Design the clocked sequential circuit using JK flip flop whose state diagram is shown below:

[CO3, 4]

 

Q. 4 Design a MOD-5 counter to count the random sequence 0, 1 3, 7, 6. Design should be circulatory to ensure that if we end in any unwanted state, the next clock pulse will reset the counter to zero.

Implement the circuit using T-flip flop.

[CO3,4]

Q. 5 Design a 4-bit bidirectional shift register with parallel load such that its mode control is as given below. (using 4 x 1 MUX)

[CO3, 4]

Mode Control		Register
S1	S0	Operation
0	0	Parallel load
0	1	No change
1	0	Shift right
1	1	Shift left

Soluhon T2.

Ques 1 Convert D flip flop into JK Flip Flop.

Solun 1

Desired Flip Flop


J	K	Q(t)	Q(t+1)	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

(1.5) Marks

J	K Q(t)			
	00	01	11	10
0	0	1	0	0
1	0	1	0	1

$$D = J \overline{Q(t)} + \overline{K} Q(t)$$

(1.5) Marks

 

(1) Mark

Ques 2 Design a two bit magnitude comparator using 1-bit comparators

Soluⁿ 2


$$(A \geq B) = x_1 \cdot A_0 \bar{B}_0 + A_1 \bar{B}_1$$

$$(A < B) = \bar{A}_1 \cdot B_1 + x_1 \bar{A}_0 B_0$$

$$(A = B) = x_1 \cdot x_0 \quad \text{where} \quad x_1 = A_1 B_1 + \bar{A}_1 \bar{B}_1$$


$$x_0 = A_0 B_0 + \bar{A}_0 \bar{B}_0$$

(1.5) Marks

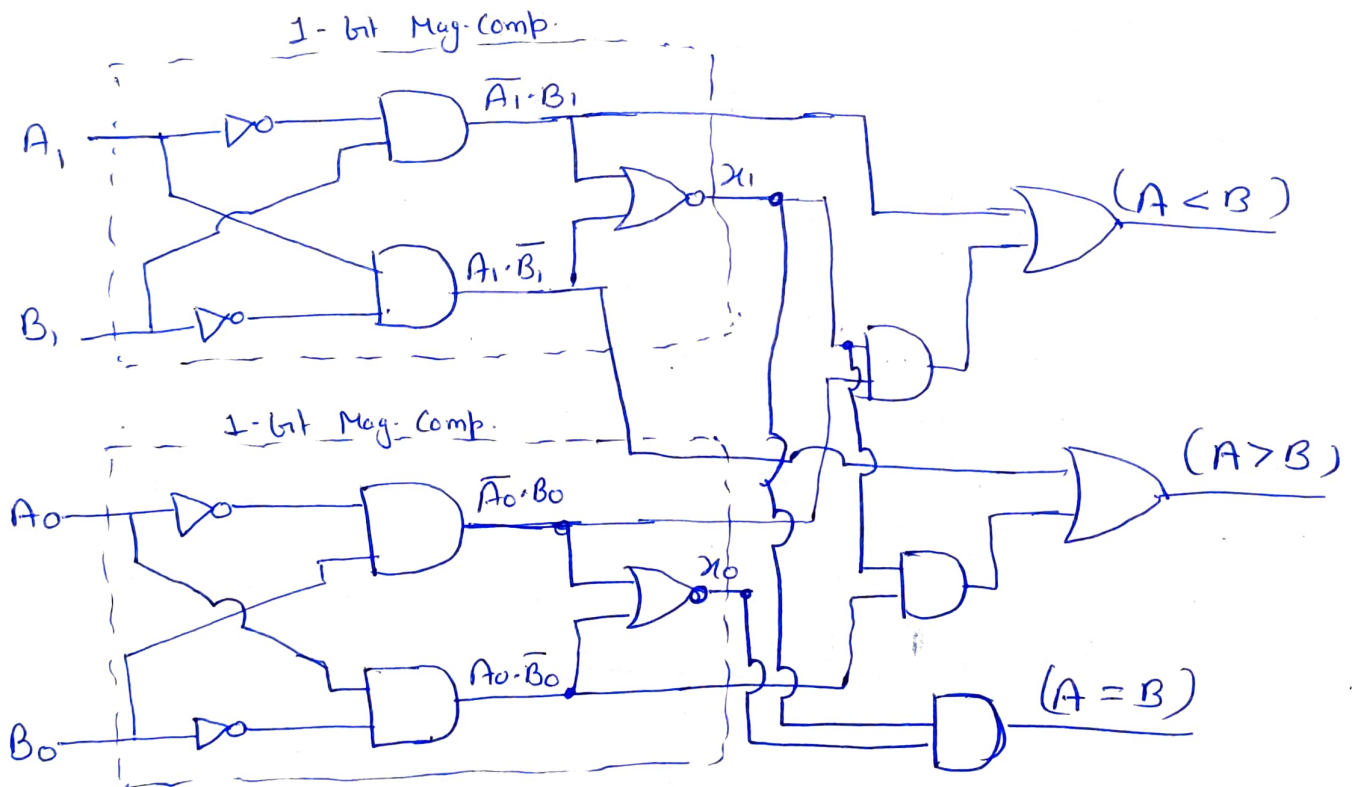

↑
(2.5) Marks

Ques 3 Design the clocked sequential circuit using JK flip flop whose state diagram is shown below

 

Solution 3

Present State		Input x	Next State		Flip Flop Input			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	x	0	x
0	0	1	0	1	0	x	1	x
0	1	0	1	0	1	x	x	1
0	1	1	0	1	0	x	x	0
1	0	0	1	0	x	0	0	x
1	0	1	1	1	x	0	1	x
1	1	0	1	0	x	0	x	0
1	1	1	0	0	x	1	x	1

└ (1) Mark

For J_A

A \ Bx	00	01	11	10
0	0	0	0	1
1	x	x	x	x

$$J_A = B\bar{x} \quad (0.5)$$

For K_A

A \ Bx	00	01	11	10
0	x	x	x	x
1	0	0	1	0

$$K_A = Bx \quad (0.5)$$


For J_B

A \ Bx	00	01	11	10
0	0	1	x	0
1	0	1	x	0

$$J_B = x \quad (0.5)$$

A \ Bx	00	01	11	10
0	x	x	0	1
1	x	x	1	0

$$K_B = A \odot x \quad (0.5)$$

 


(1) Mark.

Ques 4 Design a module-5 counter to count the random sequence 0, 1, 3, 2, 6. Design should include circuitry to ensure that if we end in any unwanted state, the next clock pulse will reset the counter to zero. Implement the circuit using T-Flop Flop.

Solⁿy

State Diagram

 

(1.5)
Marks

For T_2

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	0	0	1	0
1	1	1	0	1

$$T_2 = Q_2 Q_1 + Q_2 \bar{Q}_0 + \bar{Q}_2 Q_1 Q_0 \quad \text{--- (0.5)}$$

For T_1


$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	0	1	0	1
1	0	0	0	1

$$T_1 = Q_1 \bar{Q}_0 + \bar{Q}_2 \bar{Q}_1 Q_0 \quad \text{--- (0.5)}$$

For T_0

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	1	0	0	0
1	0	1	1	0
 
$$T_0 = \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 + Q_2 Q_0 \quad \text{--- (0.5)}$$



(1) Mark

Ques 5 Design a 4-bit bidirectional shift register with parallel load such that its mode control as given below. (using 4×1 Mux)

Mode Control		Register Operation	Color Lines
S_1	S_0		
0	0	Parallel load	→ (1) Mark
0	1	No change	→ (1) Mark
1	0	Shift Right	→ (1) Mark
1	1	Shift left.	→ (1) Mark

Soln

